


Lecture 19

RTL Design Methodology


SORTING example



Structure of a Typical Digital System

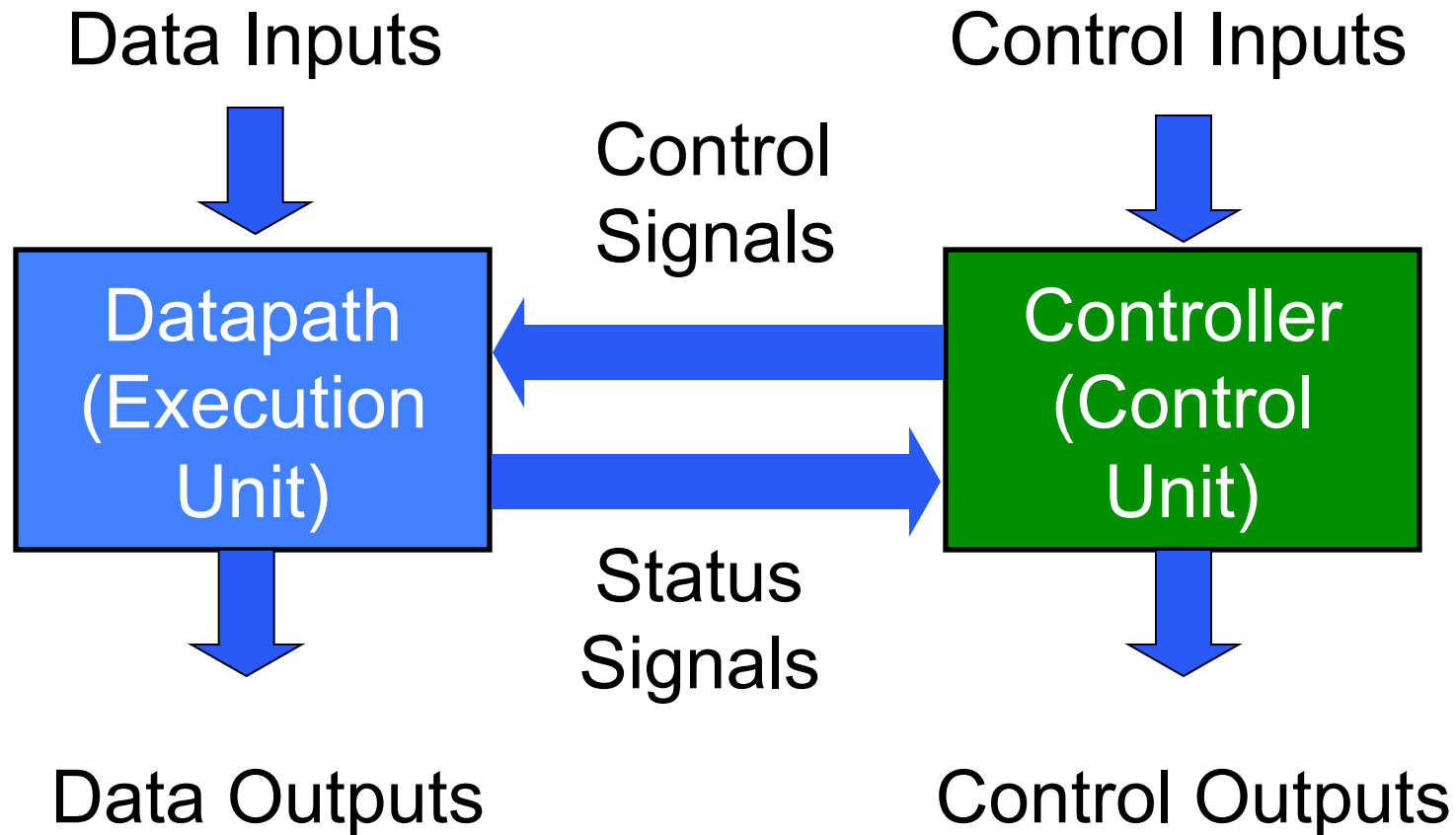

Hardware Design with RTL VHDL

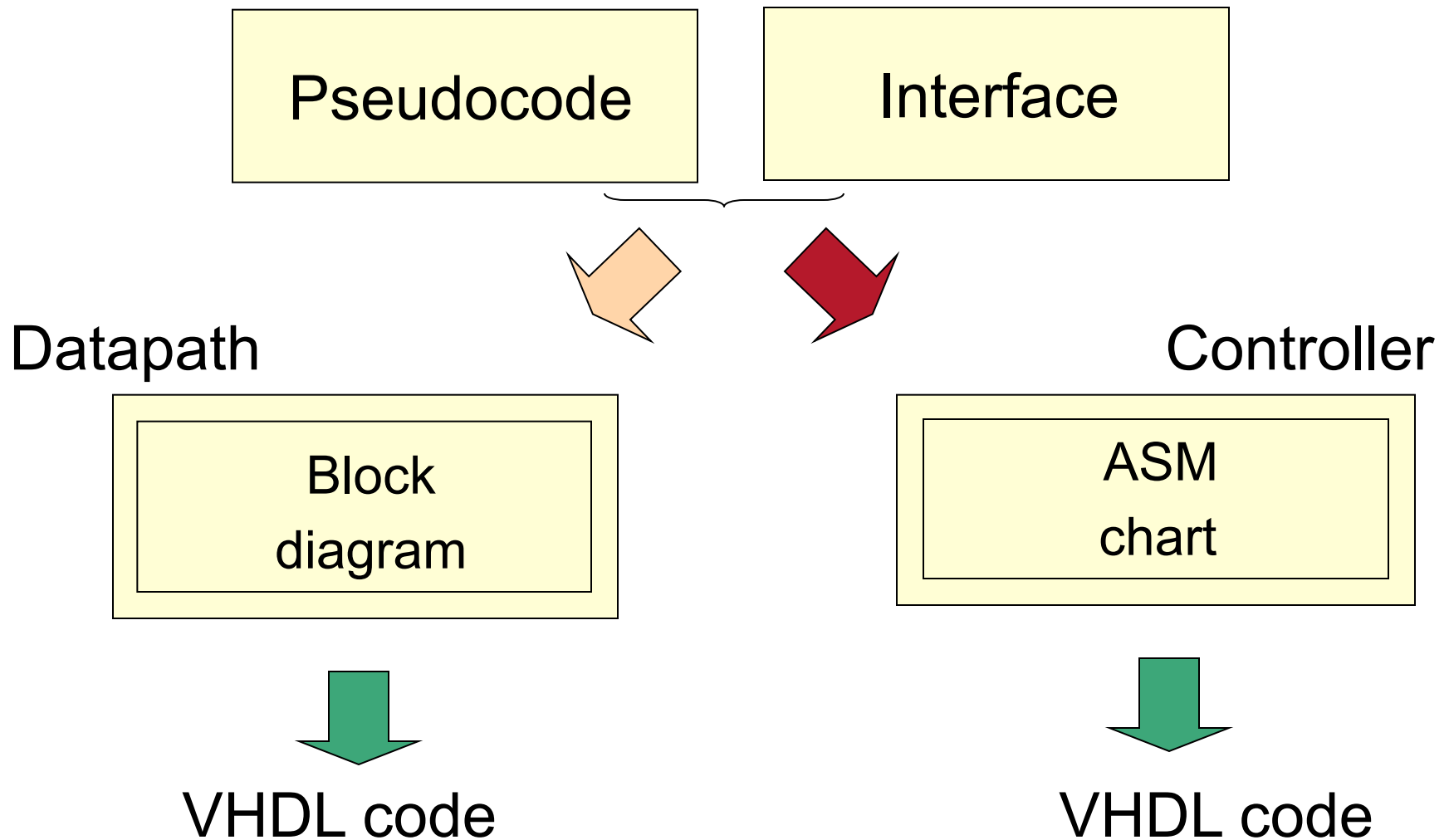

Steps of the Design Process

1. Text description
2. Interface
3. Pseudocode
4. Block diagram of the Datapath
5. Interface divided into Datapath and Controller
6. ASM chart of the Controller
7. RTL VHDL code of the Datapath, Controller, and Top-Level Unit
8. Testbench for the Datapath, Controller, and Top-Level Unit
9. Functional simulation and debugging
10. Synthesis and post-synthesis simulation
11. Implementation and timing simulation
12. Experimental testing using FPGA board

Steps of the Design Process Introduced in Class Today

1. Text description
2. Interface
3. Pseudocode
- 4. Block diagram of the Datapath**
- 5. Interface divided into Datapath and Controller**
- 6. ASM chart of the Controller**
7. RTL VHDL code of the Datapath, Controller, and Top-level Unit
8. Testbench for the Datapath, Controller, and Top-Level Unit
9. Functional simulation and debugging
10. Synthesis and post-synthesis simulation
11. Implementation and timing simulation
12. Experimental testing using FPGA board

SORTING example


High Performance

CoolClock

Low Power

DataCache

Sorting - Required Interface

 


Sorting - Required Interface

Port	Width	Meaning
Clock	1	System clock
Resetn	1	System reset – clears internal registers. Active low.
DataIn	N	Input data bus
RAdd	L	Address of the internal memory where input data is stored
WrInit	1	Synchronous write control signal
s	1	Operating mode: 0 = initialization, 1 = computations.
Rd	1	Read enable. 0 = high impedance on the output bus, 1 = valid output on the output data bus.
DataOut	N	Output data bus used to read results
Done	1	Asserted when all results are ready


Simulation results for the sort operation (1)

Loading memory and starting sorting

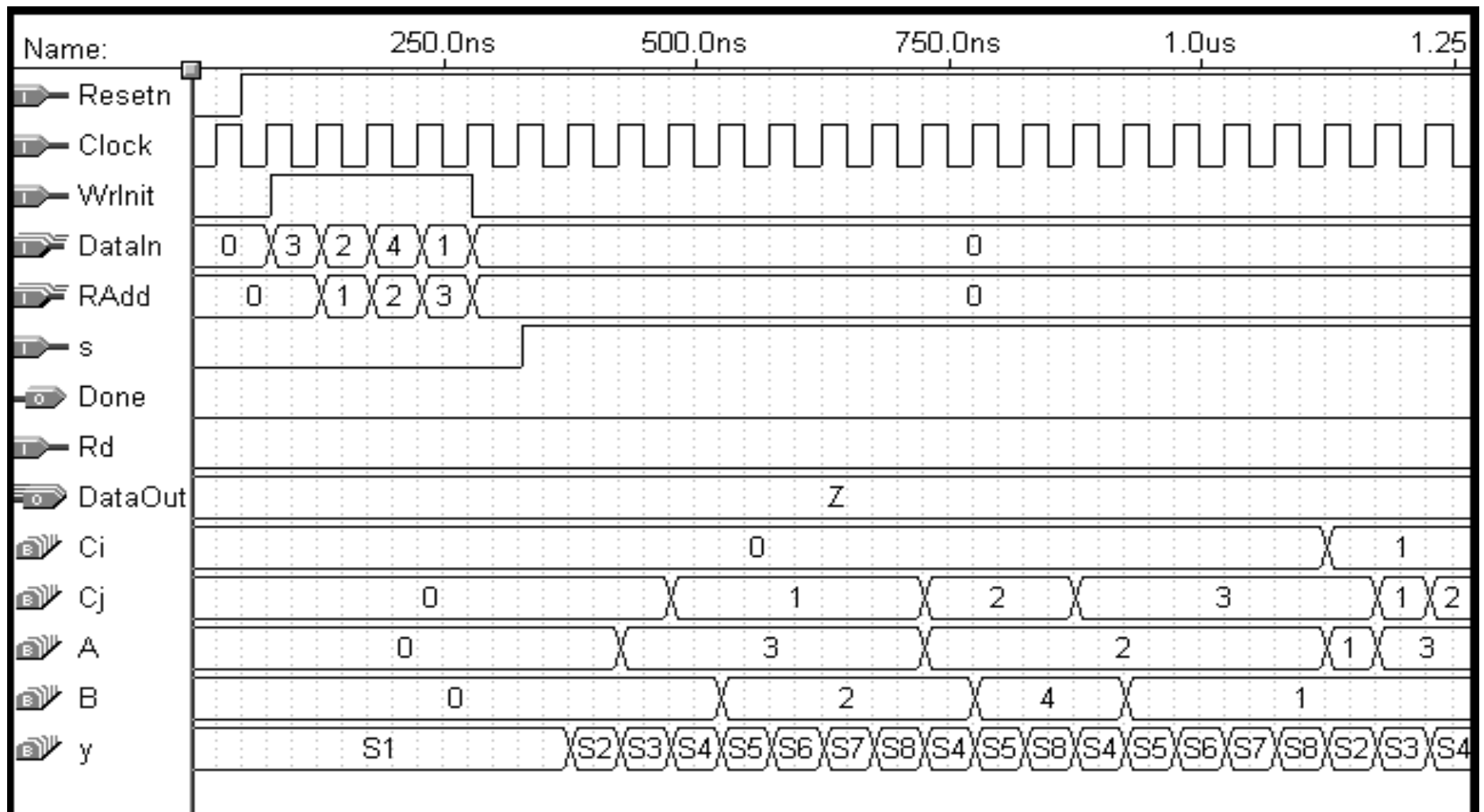

Simulation results for the sort operation (2)

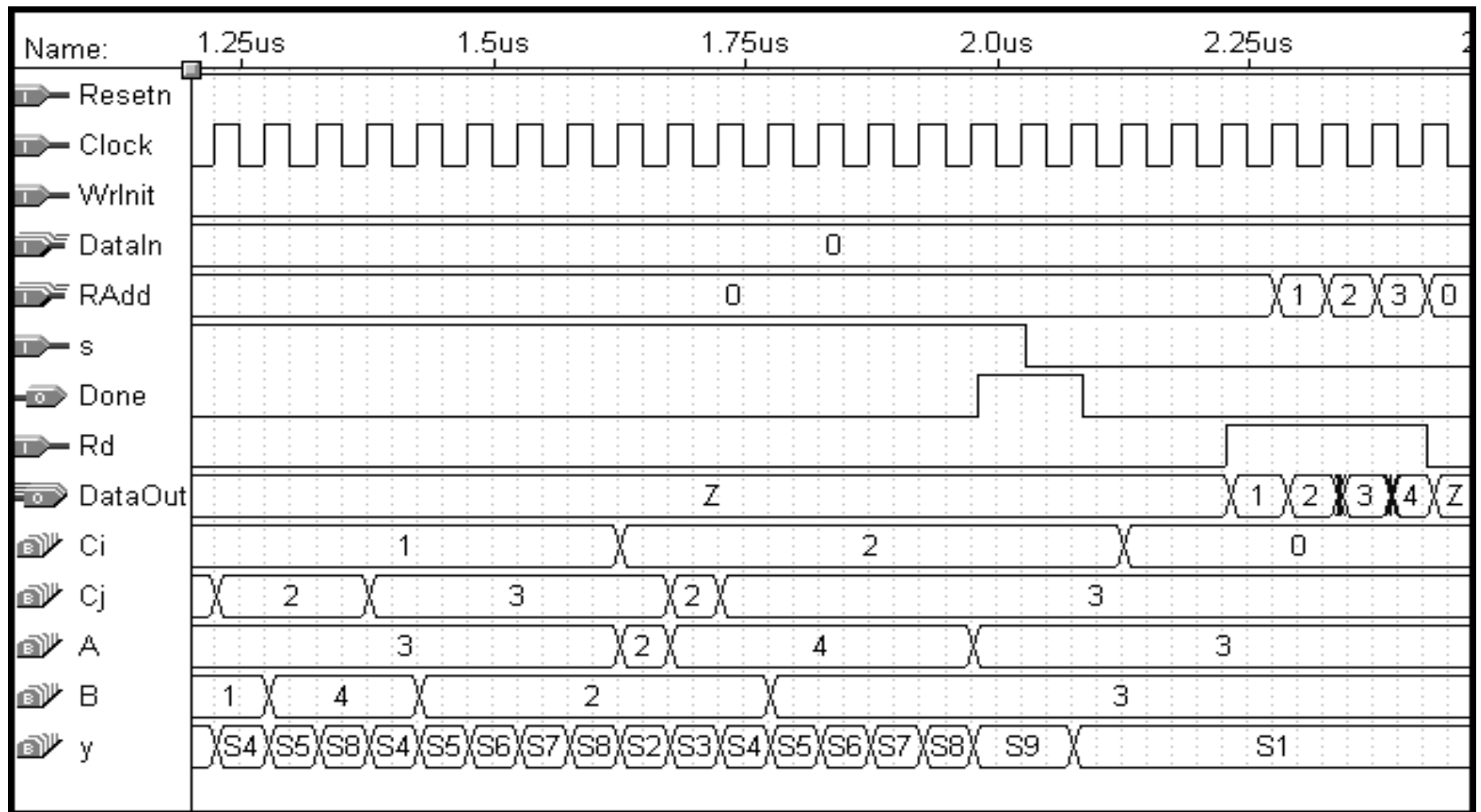Completing sorting and reading out memory



Sorting - Example

		During Sorting						After sorting
Before sorting		i=0 j=1	i=0 j=2	i=0 j=3	i=1 j=2	i=1 j=3	i=2 j=3	
Address								
0	3	3	2	2	1	1	1	1
1	2	2	3	3	3	3	2	2
2	4	4	4	4	4	4	4	3
3	1	1	1	1	2	2	3	4

Legend:

position of memory
indexed by i

M_i

position of memory
indexed by j

M_j

Pseudocode

FOR k = 4

```
[load input data]
wait for s=1
for i = 0 to 2 do
    A = Mi ;
    for j = i + 1 to 3 do
        B = Mj ;
        if B < A then
            Mi = B ;
            Mj = A ;
            A = Mi ;
        endif ;
    endfor;
endfor;
Done
wait for s=0
[read output data]
go to the beginning
```

FOR any k ≥ 2

```
[load input data]
wait for s=1
for i = 0 to k-2 do
    A = Mi ;
    for j = i + 1 to k - 1 do
        B = Mj ;
        if B < A then
            Mi = B ;
            Mj = A ;
            A = Mi ;
        endif ;
    endfor;
endfor;
Done
wait for s=0
[read output data]
go to the beginning
```

Pseudocode

```
wait for s=1
for i=0 to k-2 do
  A = Mi
  for j=i+1 to k-1 do
    B = Mj
    if A > B then
      Mi = B
      Mj = A
      A = Mi
    end if
  end for
end for
Done
wait for s=0
go to the beginning
```


SORTING solutions

High Performance

CoolClock

Low Power

DataCache

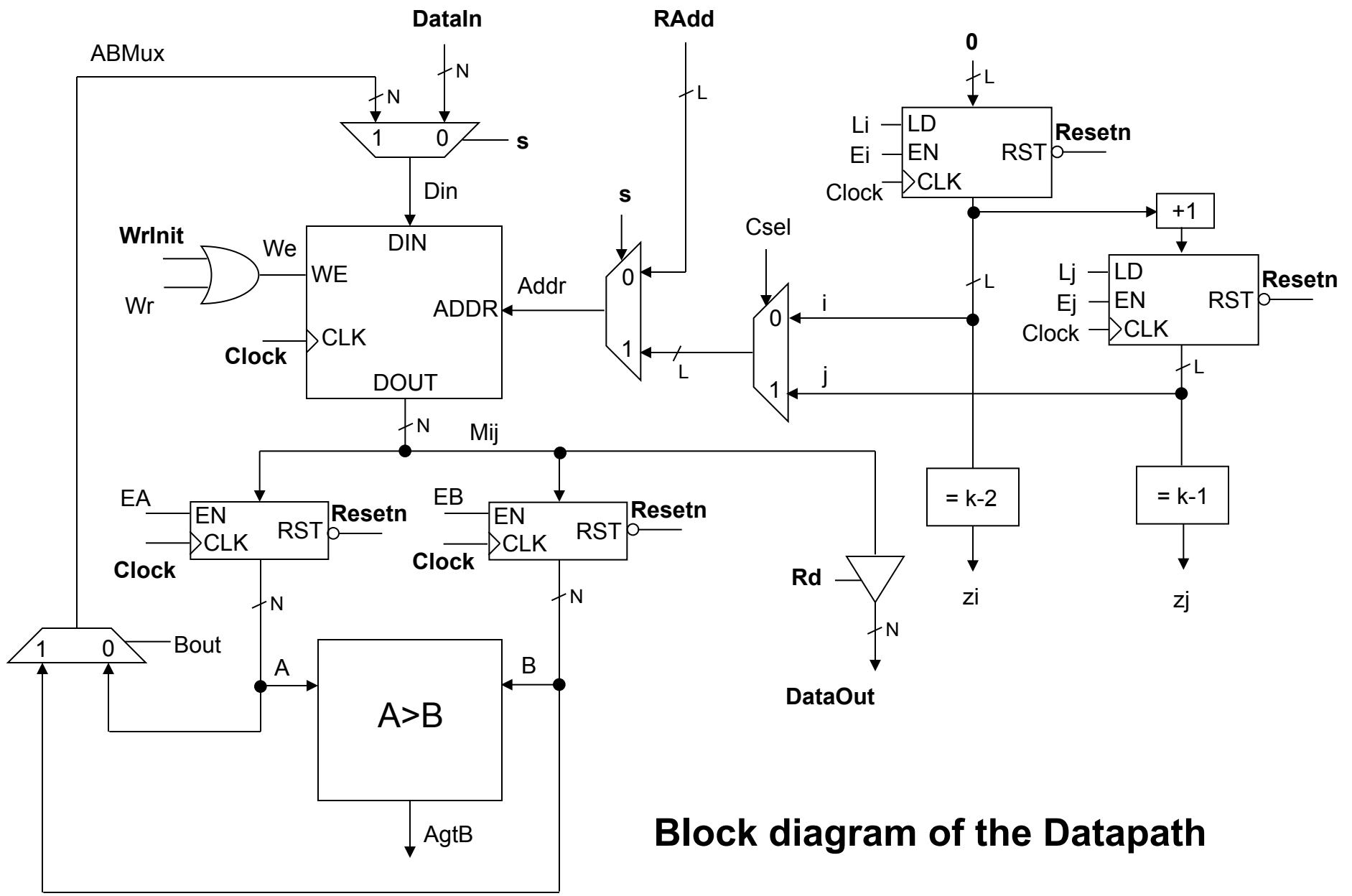

Block diagram of the Datapath

Interface with the division into Datapath and Controller

